



university of
 groningen

Computer Architecture 2023-24 (WBCSo10-05)

Lecture 3: Digital Logic Structures

Reza Hassanpour
r.zare.hassanpour@rug.nl



Topics

- › Digital Logic
- › Logic Gates
- › Combinational Logic
 - Multiplexer
 - Decoder
 - Adder
- › Sequential Logic
 - S-R Latch
 - D Latch



Digital Computers

- › We use the term **digital computer** to refer to a device that performs a **sequence of computational steps** on data items that have **discrete values**.
- › **Digital logic** is the **manipulation of binary values** through technology that uses **circuits and logic gates** to construct the implementation of computer operations.



Boolean Logic

- › Mathematical basis for digital circuits
- › Three basic functions: *and*, *or*, and *not*

A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

A	NOT A
0	1
1	0



Digital Logic

- › Is the implementation of Boolean functions with transistors where:
 - Five volts represents Boolean 1 (true)
 - Zero volts represents Boolean 0 (false)
- › Voltage:
 - Quantifiable property of electricity in the form of the pressure that pushes charged electrons (current) through a conducting loop.
 - Unit: volt
- › Current
 - Measure of electron flow along a path
 - Unit: ampere (amp)




Voltage/Current Analogy

- › Voltage is analogous to water pressure
- › Current is analogous to flowing water
- › Water can have
 - High pressure with little flow
 - Large flow with little pressure

Transistor: Building Block of Computers

 - › Microprocessors contain billions of transistors
 - Intel Broadwell-E5 (2016): 7 billion
 - IBM Power 9 (2017): 8 billion
 - Intel Ponte Vecchio (2021): 100 billion (is it a CPU?)
- › Logically, each transistor acts as a **switch**
- › Combined to implement **logic functions**
 - AND, OR, NOT, ...



Combined to build **higher-level structures**


- Adder, multiplexer, decoder, register, ...

Combined to build **processors**

A Simple Switch Circuit

- › A wall switch determines whether current flows through the light bulb

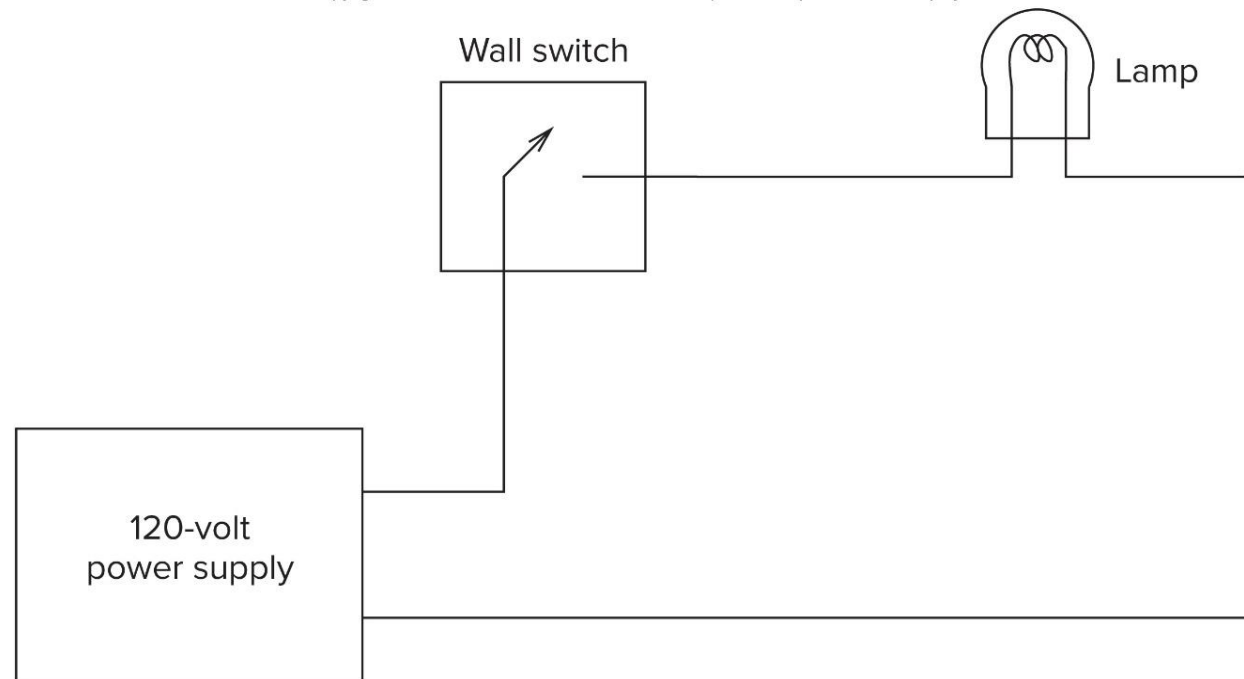Copyright © McGraw-Hill Education. Permission required for reproduction or display.




- › If switch is closed, current flows, lamp is **ON**, voltage across lamp is **non-zero**
- › If switch is open, no current flows, lamp is **OFF**, voltage across lamp is **zero**

Transistor = Voltage-Controlled Switch 1

- › Figure shows an **N-type** transistor
When Gate voltage is **positive**, relative to Source, transistor acts as a short circuit: a **closed** switch
- › When Gate voltage is **zero** (or negative), relative to Source, transistor acts as an open circuit: an **open** switch

 
Copyright © McGraw-Hill Education. Permission required for reproduction or display.



Transistor = Voltage-Controlled Switch 2

- › Consider the circuit below. The bar at the top represents the high voltage rail and the triangle at the bottom represents ground (0V)

 Copyright © McGraw-Hill Education. Permission required for reproduction or display.



- › **When Gate = +1.2V, what happens?**


- Gate-to-source voltage > 0
- Transistor = closed switch
- Current flows, lamp is **ON**

- › **When Gate = 0V, what happens?**

- Gate-to-source voltage = 0
- Transistor = open switch
- No current flows, lamp is **OFF**

Transistor = Voltage-Controlled Switch 3

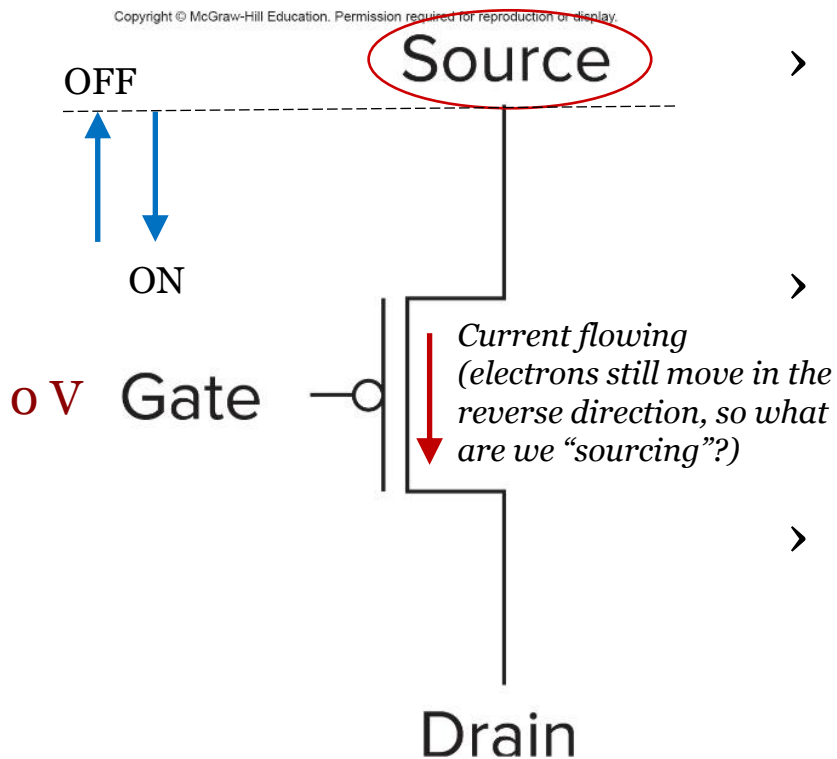- › A different type of transistor is shown below, the **P-type** transistor. Notice the little "bubble" on the gate



- › When Gate voltage is **zero** (or negative), relative to Source, transistor acts as a short circuit: a **closed** switch
- › When Gate voltage is positive, relative to Source, transistor acts as an open circuit: an **open** switch
- › NOTE: This behavior is the opposite of the N-type. Behavior is complementary

- › We use both N-type and P-type transistors together to implement logic gates. This is known as **CMOS** or Complementary MOS logic




Logic Gate

- › Transistors have two possible states:
 - current is flowing or
 - no current is flowing.
- › Therefore, circuits are designed using a two-valued mathematical system known as Boolean algebra.
- › A **logic gate** is a **circuit implementation of Boolean function**.
- › Signals are the voltages.

NOT Gate (Inverter)

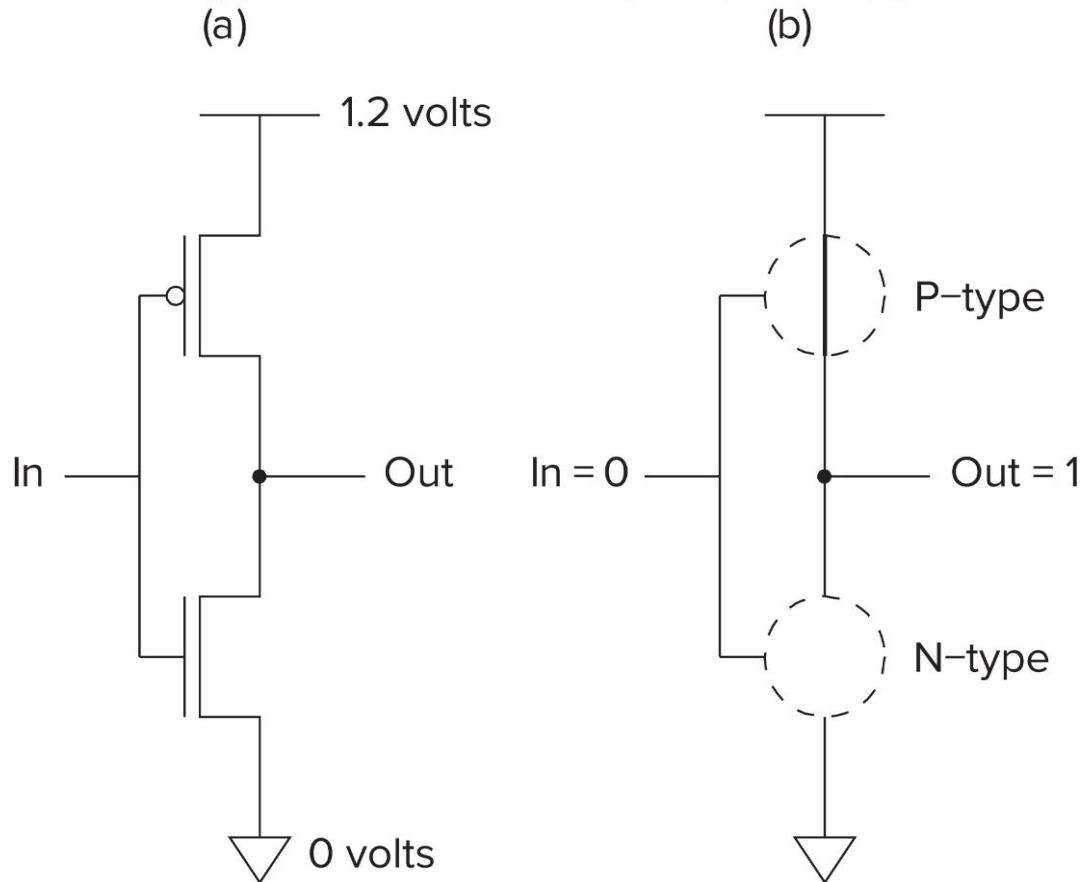Copyright © McGraw-Hill Education. Permission required for reproduction or display.



- › Example:
- › When input = 0, P-type transistor turns on and N-type transistor turns off. Output is connected to +1.2V, so output = 1
- › Logic gate is described using a **truth table**

Input	Output
0	1
1	0


NOR Gate

› When either input is 1, output is 0

- › Example:
- › When B = 1, N-type transistor turns on and output (C) is connected to GND. Both inputs must be 0 to connect C to +1.2V.


Copyright © McGraw-Hill Education. Permission required for reproduction or display.

(a)

 

Copyright © McGraw-Hill Education. Permission required for reproduction or display.

(b)

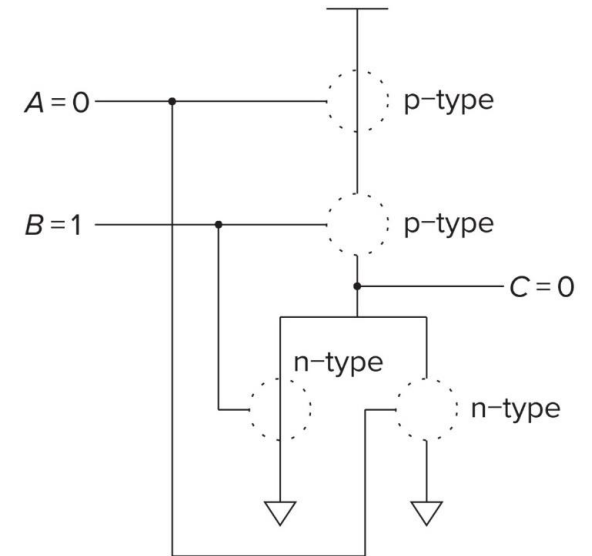


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

$$C = \text{NOT}(A \text{ OR } B)$$


OR Gate

- When either input is 1, output is 1
- Add NOT after NOR

 Copyright © McGraw-Hill Education. Permission required for reproduction or display.



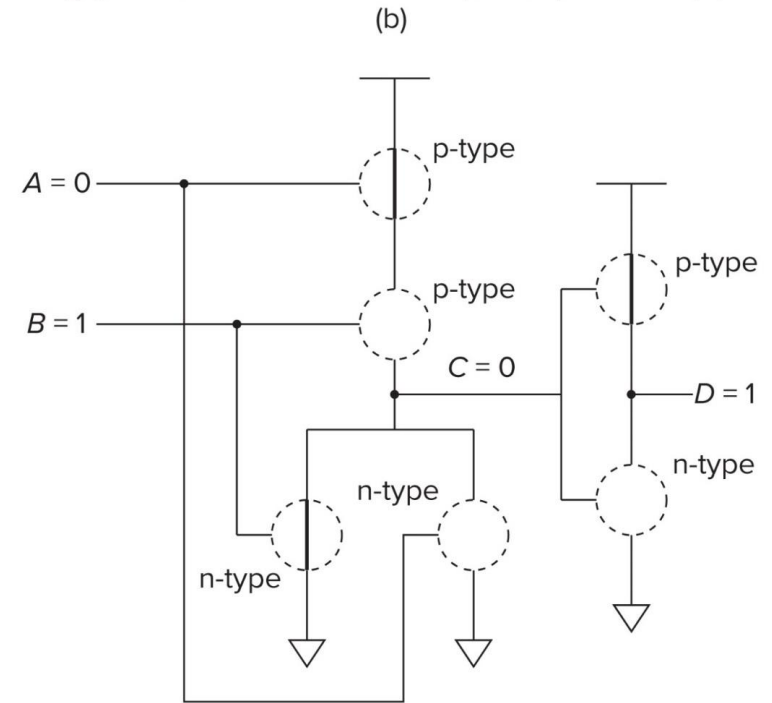Copyright © McGraw-Hill Education. Permission required for reproduction or display.




A	B	C	D
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

NAND and AND Gates

- › NAND: When any input is 0, output is 1
- AND: When all inputs are 1, output is 1

Copyright © McGraw-Hill Education. Permission required for reproduction or display.

(a)

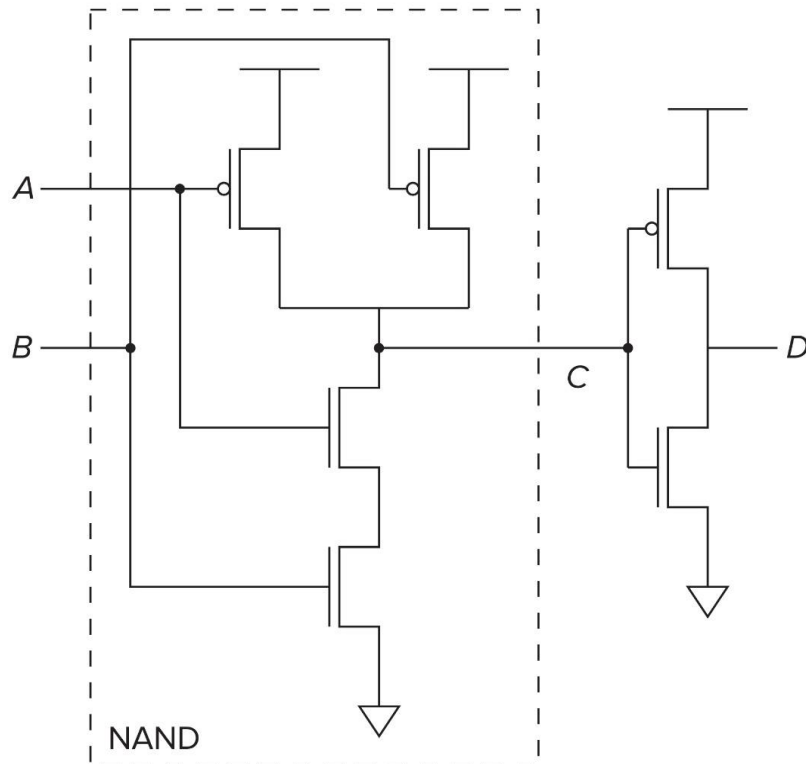

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

› NAND


A	B	D
0	0	0
0	1	0
1	0	0
1	1	1

› AND


Standard Symbols for Logic Gates

- › Instead of drawing the circuit diagram, we can **abstract** these logic gates and give each a symbol. The bubble indicates inversion (NOT).

 
Copyright © McGraw-Hill Education. Permission required for reproduction or display.




(a) Inverter

 


(b) AND gate

 

(c) OR gate

 

(d) NAND gate

 


(e) NOR gate

Gates with more than one input

- › Notion of AND and OR generalizes to more than two inputs.
- › AND: output = 1 if ALL inputs are 1
- › OR: output = 1 if ANY input is 1

(a)

<i>A</i>	<i>B</i>	<i>C</i>	OUT
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

Challenge: Draw the CMOS circuit for a 3-input AND gate
What about 4-input NOR gate?

Building Logic Circuits from Gates


- › To build more complex logic functions, we create circuits using the basic logic gates
- › **Combinational** Logic Circuits
 - Output depends only on the current input values
 - Stateless -- no "memory" of the past
- › **Sequential** Logic Circuits
 - Output depends on both past and current input values
 - "remembers" inputs from the past
 - **Example:** output = 1 if we see four zero inputs in a row

Combinational Logic Circuits

- › We need **both** combinational and sequential circuits to build a computer
- › First, we will introduce three useful combinational circuits:
- › **Decoder**: recognizes specific bit patterns
- › **Multiplexer**: chooses among various inputs
- › **Adder**: performs addition on unsigned or 2's complement integers

Decoder

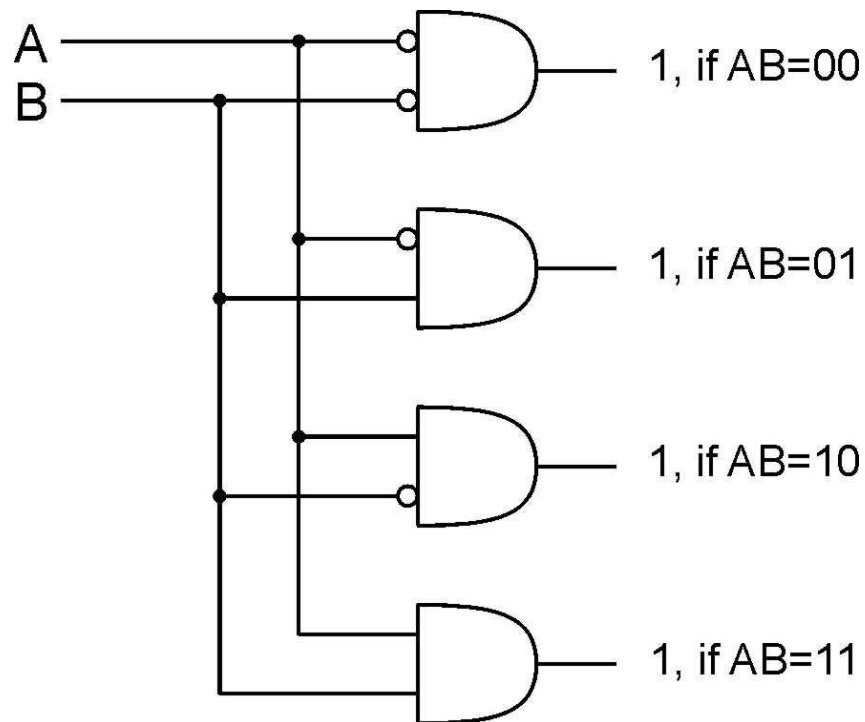
- › A decoder has n inputs and 2^n outputs
- › Each output corresponds to one possible input combination
- › Exactly one output will be 1, and all others will be 0




2-bit decoder

*Useful for converting
encoded values (integers)
into a set of control signals*

 Example: Using Decoders to Display Numbers on a Seven-Segment Display




Decoding BCD = 3

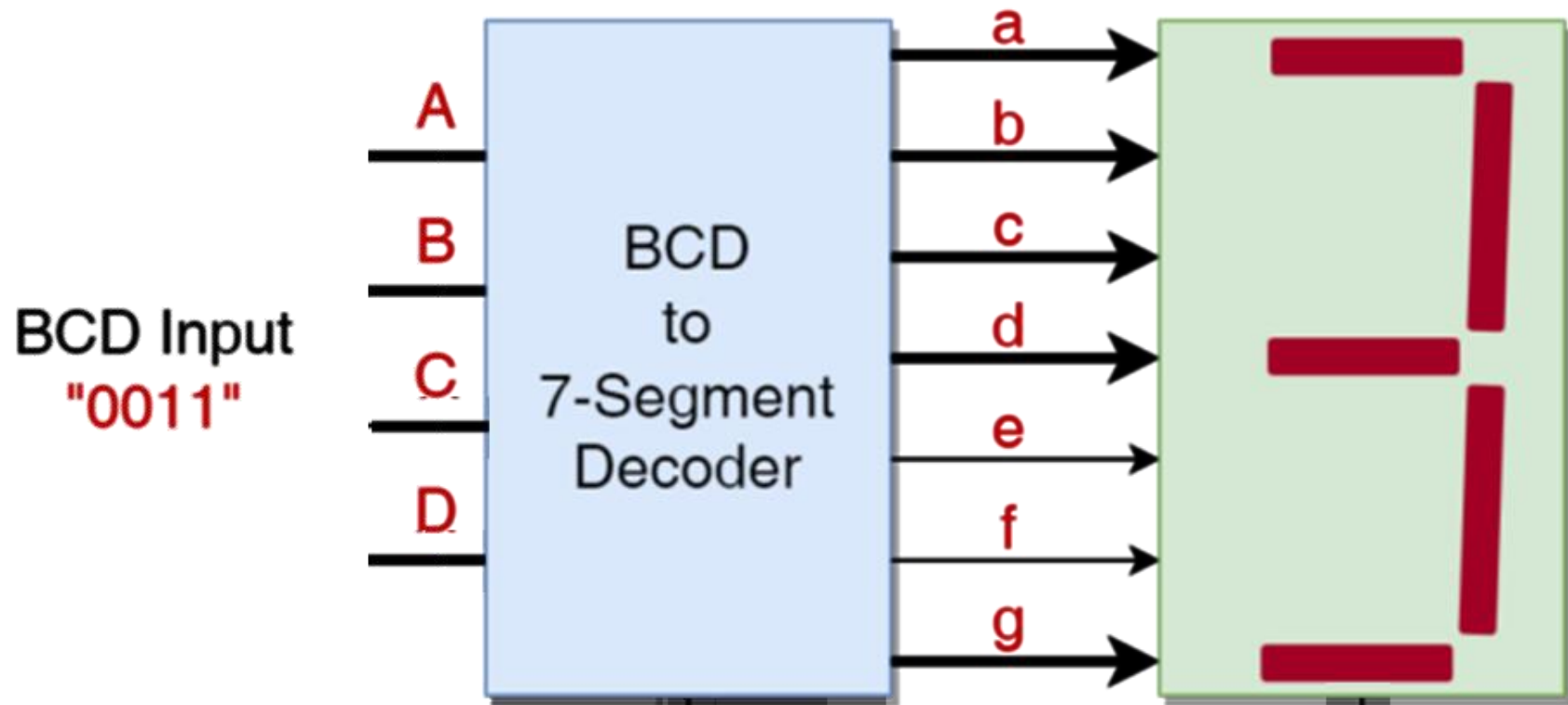


Turn On Segment e

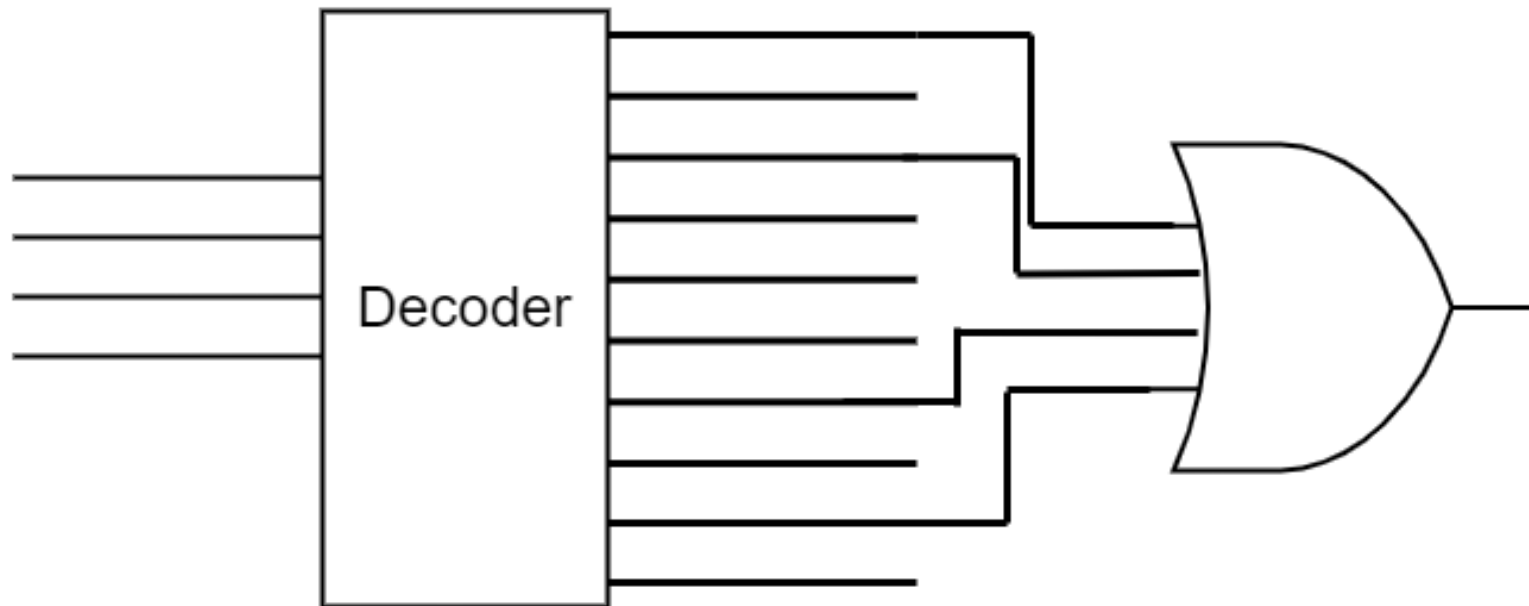e should be turned on when the input is 0, 2, 6, or 8




Encoder

 - › An encoder performs the opposite of a decoder.
- › Only one input of its n inputs is 1 each time.
- › The output ($\log_2 n$) is the binary representation of the input.




Multiplexer (Mux)

 - › A mux has 2^n data inputs, n select inputs, and one output
- › The select bits are used to "choose" one of the data inputs to flow through to the output




4-to-1 mux
4 input bits,
2 select bits

 

- › *This is the standard symbol for a mux. S is a two-bit signal*
- › *S_1 is the most significant bit, and S_0 is the least significant bit*

Full Adder (1-bit binary addition)

 
- A full adder represents one column in a binary addition operation. A and B are the bits to be added. C_{in} is the carry-in from the previous column (from the right). There are two outputs: S = sum, C_{out} = carry-out (to the next column).



C_{in}	A	B	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

N-bit Adder

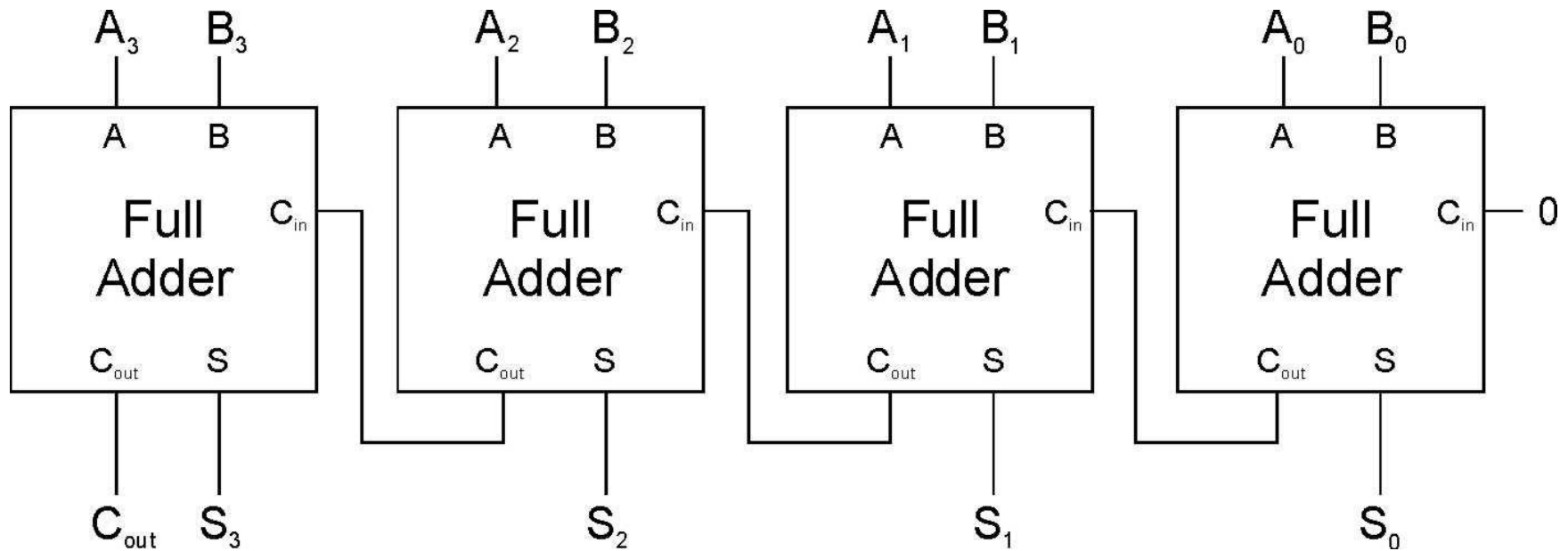- › Feed C_{out} from one bit into C_{in} of the next bit...



Q: would all additions take the same time?

Full Subtractor Using an 8 by 1 Multiplexer

› Subtracting binary digits yields:

- $0 - 0 = 0$
- $1 - 0 = 1$
- $0 - 1 = 1$, borrow = 1
- $1 - 1 = 0$


› Therefore, we will have:

A	B	C _{in}	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

Full Subtractor Using an 8 by 1 Multiplexer

- › The input to the multiplexer is either logical 1, or logical 0.
- › Selecting one of these inputs in the output will depend on the bits to be subtracted, and carry in.
- › One multiplexer will provide the difference, and a second multiplexer will give the borrow bit.

 
Full Subtractor Using an 8 by 1 Multiplexer



B_{in}	A	B	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1



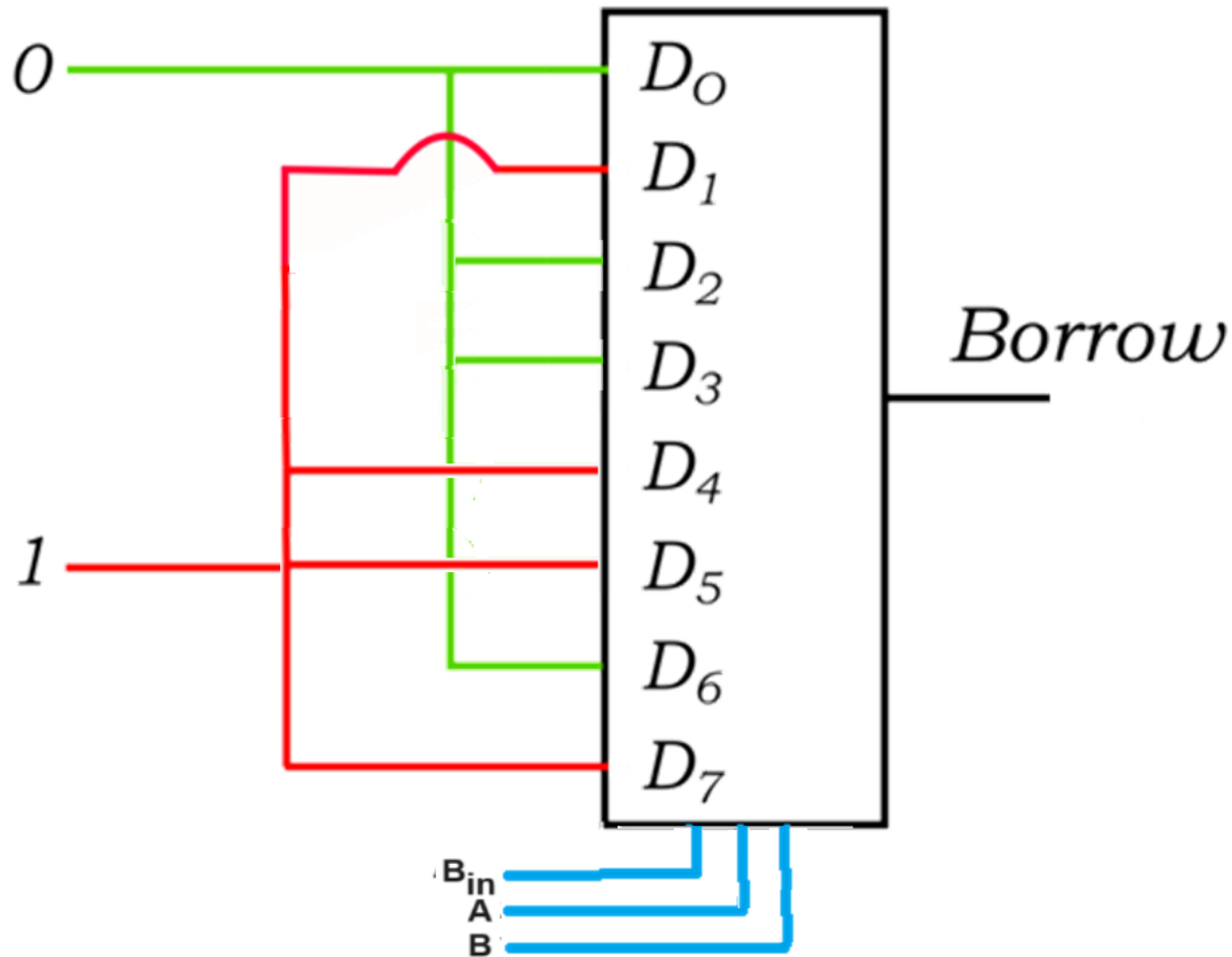Full Subtractor Using an 8 by 1 Multiplexer





Bin	A	B	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

Sequential Logic Circuits

- › Output depends on previous state(s)
- › Must store previous information in order to act on it
- › Example: ticket counter
 - When input is 1, output the "next" count: 0, 1, 2, 3, 4, 5, ...
 - Output depends on stored data (the current count) plus the input
- › Requires storage element (memory)
- › Will be used to implement "state machines" that perform a prescribed sequence of actions, depending on inputs

Storing One Bit: R-S Latch

  
- › A latch uses feedback to store a bit of information. In the circuit below, inputs R and S are both 1. The output may be either 0 or 1.
- › **NOTE:** This is different than combinational logic -- different possible outputs for a particular input.




As long as $R = S = 1$, the output is stable. It either stays 0 or stays 1. This is known as the **quiescent** state. The circuit "remembers" this data.

Clearing the latch: $R = 0$

 - › To force the output (the stored data) to zero, set $R = 0$ and $S = 1$




RESET

 


- › Once the latch is cleared, make $R = S = 1$ to remember the data

Setting the latch: $S = 0$

 - › To force the output (the stored data) to one, set $R = 1$ and $S = 0$



SET

 

- › *Once the latch is set, make $R = S = 1$ to remember the data*

R-S Latch Summary

$R = S = 1$

Hold current value in latch

$R = 0, S = 1$

Clear/reset latch (value = 0)

$R = 1, S = 0$

Set latch (value = 1)

R	S	Q'
0	0	<i>invalid</i>
0	1	0
1	0	1
1	1	Q

Q' is output. Q is previous output


What about $R = 0, S = 0$?

Both outputs = 1, final state determined by electrical properties of the gates.

Don't do it!!! This set of inputs is prohibited and should never occur during the operation of the latch.

D-Latch: Simpler Control for One-Bit Latch

 - › D = data input, WE = write enable
- › When WE = 0, latch output does not change (D is irrelevant)
- › When WE = 1, latch output = D



- › **NOTE:** This uses an R-S latch. R and S will never both be zero



Summary

- › Digital logic is the implementation of Boolean functions with transistors.
- › Combination logic is a circuit where the output depends on the input(s) only.
 - Multiplexer
 - Decoder
 - Full adder/subtractor
- › Sequential logic is a circuit where the output depends on the input and the current state.
- › Both combinational and sequential logic circuits are required to design a digital computer.



university of
 groningen

Questions?