



university of
 groningen

Computer Architecture 2023-24 (WBCSo10-05)

Lecture 4: Sequential Logic


Reza Hassanpour
r.zare.hassanpour@rug.nl

Introduction

- › The output from combinational logic circuits depends only on their inputs.
- › Digital computers need to store data/state, and decide the output based on inputs and stored data/state.
- › Sequential logic circuits the output depends upon present as well as past input.
- › **Q:** How can we store the results we received in the past?

Decoder (recap)

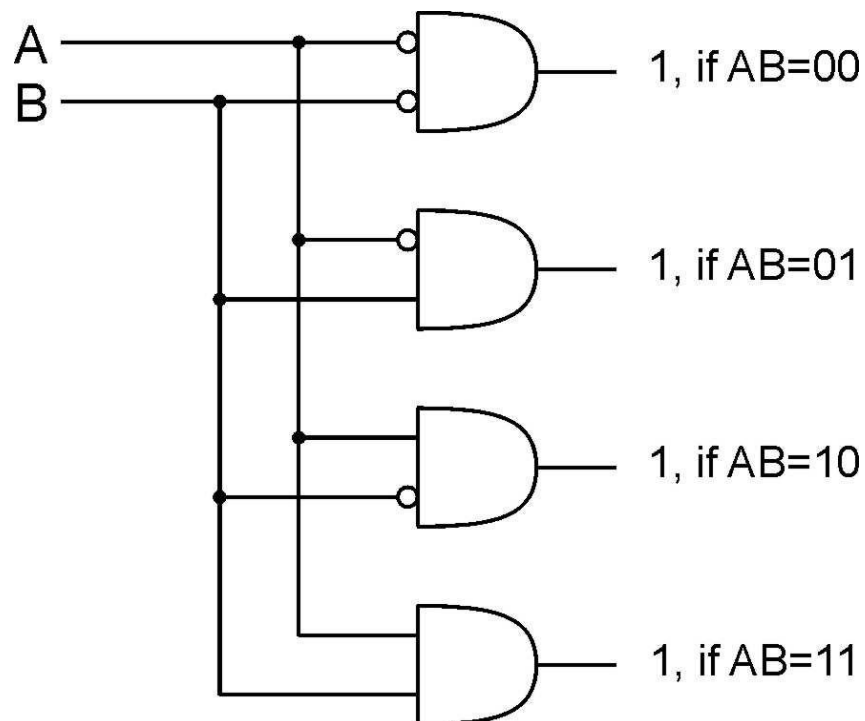- › A decoder has n inputs and 2^n outputs
- › Each output corresponds to one possible input combination
- › Exactly one output will be 1, and all others will be 0




2-bit decoder


*Useful for converting
encoded values (integers)
into a set of control signals*

Multiplexer (Mux) (recap)

 - › A mux has 2^n data inputs, n select inputs, and one output
- › The select bits are used to "choose" one of the data inputs to flow through to the output




4-to-1 mux
4 input bits,
2 select bits

 

- › *This is the standard symbol for a mux. S is a two-bit signal*
- › *S_1 is the most significant bit, and S_0 is the least significant bit*




Full Adder (1-bit binary addition) (recap)

 - › A full adder represents one column in a binary addition operation. A and B are the bits to be added. C_{in} is the carry-in from the previous column (from the right). There are two outputs: S = sum, C_{out} = carry-out (to the next column).



| C_{in} | A | B | S | C_{out} |
|----------|---|---|---|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |


Decoder (more)

   

| A | B | X | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

- › What are X and Y?
- › What if we name $X = S$ (sum) and $Y = C_{out}$?
- › This is a combinational circuit called *half-adder*
- › Can we also make a full-adder with a decoder?


Multiplexer (Mux) (more)

 

- › What function is implemented here?
- › This is a combinational circuit (inputs and select lines are “equivalent”)!
- › Question: how many Select inputs will an 8:1 MUX have?

Sequential Logic Circuit: Finite State Machine

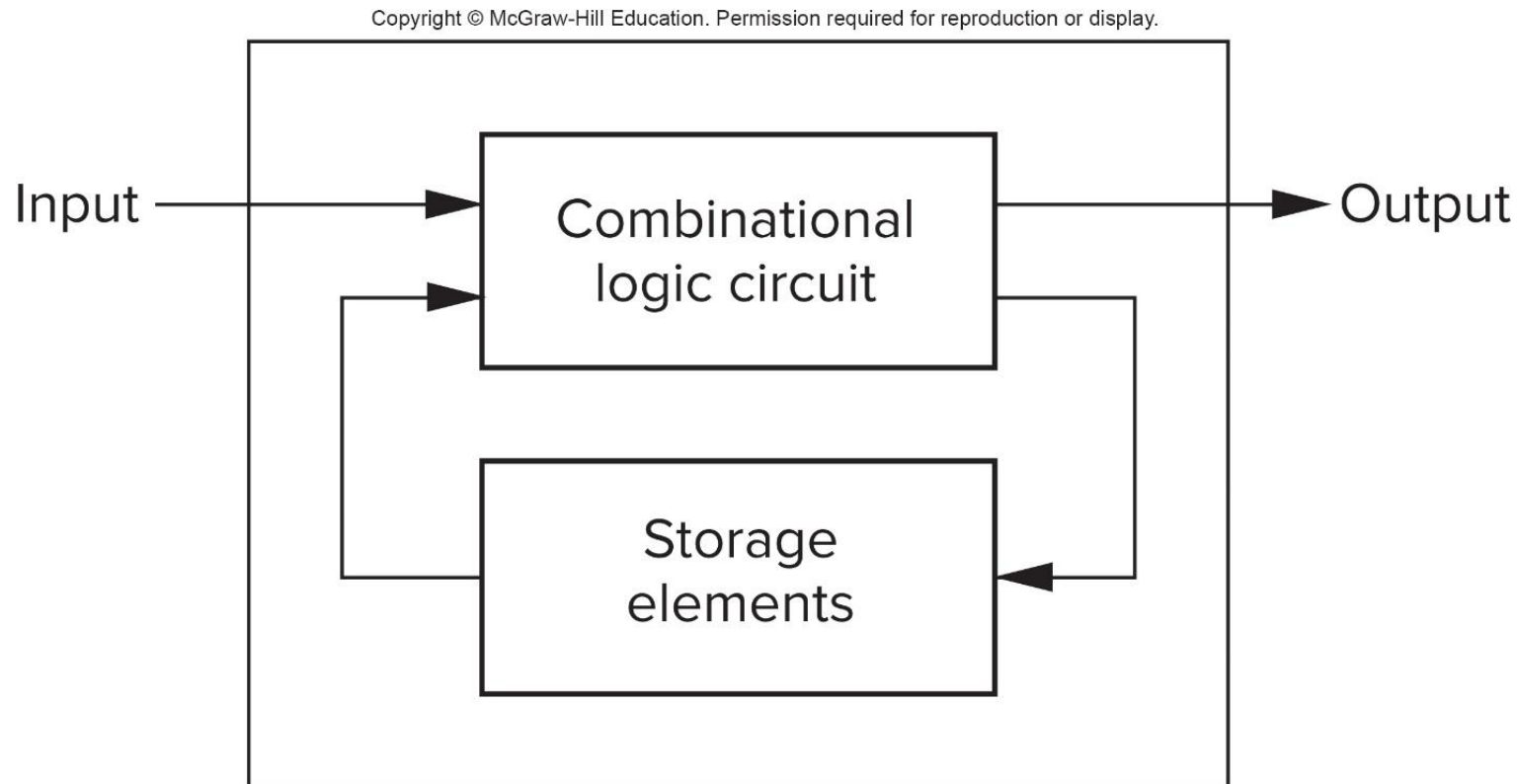- › Uses both combinational logic and storage
- › "Remembers" state, computes output (and new state) depending on previous state and new input data




What is State?

- › The **state** of a system is a **snapshot** of **all the relevant data** that describes the system
- The state of a basketball game can be represented by the scoreboard: Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board

 Example: A Combination Lock

Copyright © McGraw-Hill Education. Permission required for reproduction or display.

- › Output (lock open / closed) depends on a sequence of actions
- › For example, R-13, L-22, R-3




(a)

- › Four States:
 - › **A:** The lock is **not open**, and no relevant operations have been performed
 - › **B:** The lock is **not open**, and the user has completed the **R-13** operation
 - › **C:** The lock is **not open**, and the user has completed **R-13**, followed by **L-22**
 - › **D:** The lock is **open**. (The user completed **R-13**, **L-22**, and **R-3**)

State Diagram

 - › Description of a state machine
- › Shows all states (nodes), output value for each state (value in node), transitions (edges) between states for different input values (edge labels)




*The output value is not shown
in this example*

Finite State Machine: Definition

- › A finite state machine (FSM) is a description of a system with the following elements:
 1. A finite set of states
 2. A finite number of external inputs
 3. A finite number of external outputs
 4. An explicit specification of all state transitions
 5. An explicit specification of what determines each output value
- › A state diagram is one representation of an FSM
 - Inputs trigger state transitions
 - An output value is associated with each state (or with each transition in some specifications)

Another Example: Drink Machine

 - › Suppose you have an old drink machine that accepts nickels and dimes. Inserting 15 cents will unlock the drink dispenser.




- › A: Open -- one drink can be removed
- › B: User has inserted five cents
- › C: User has inserted ten cents
- › D: Locked, no coin has been inserted

Implementing a Finite State Machine

- › Combinational Logic -- given current state and input, what is the next state and output?
- › Storage Elements -- stores state bits until next cycle

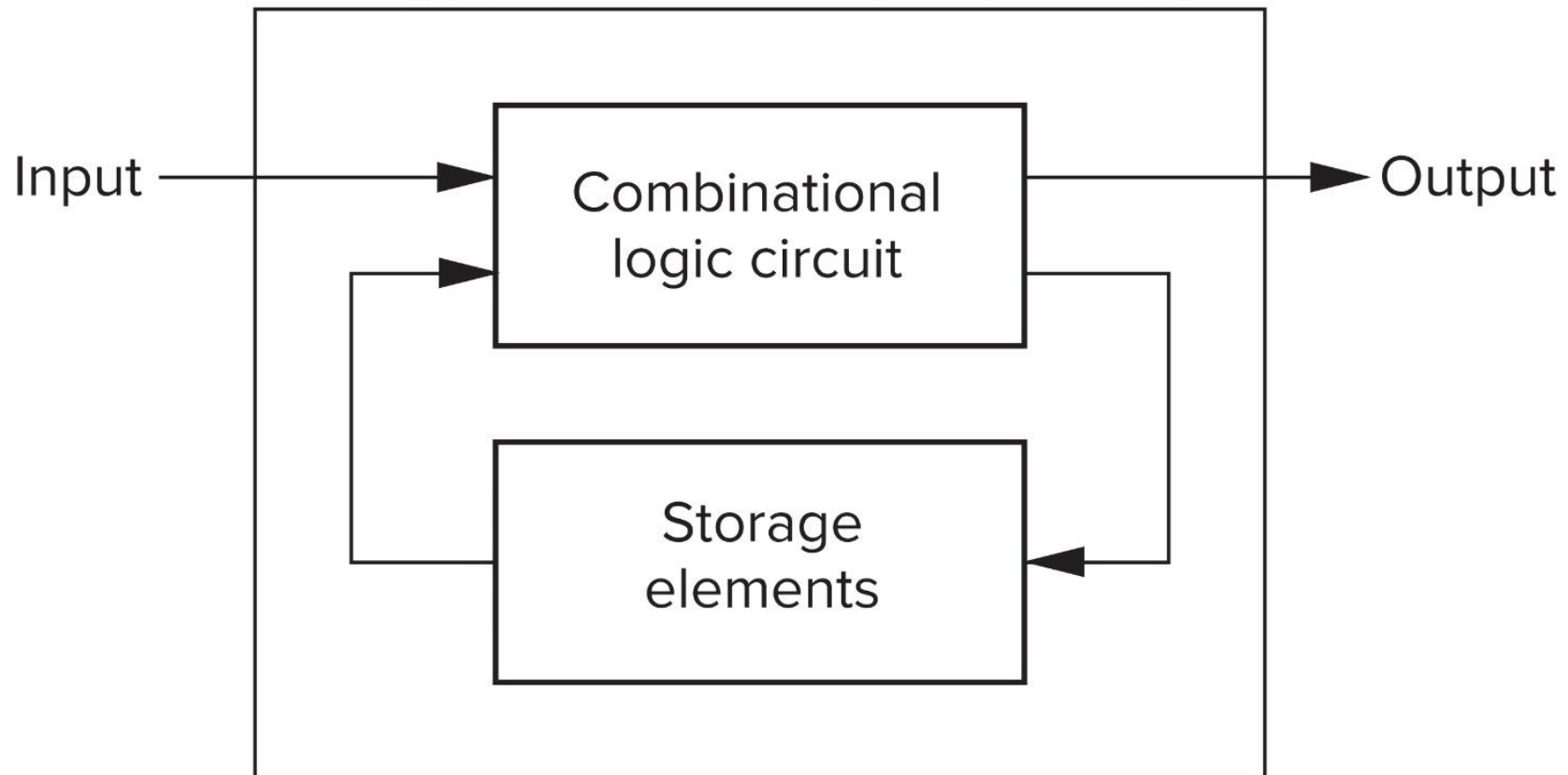
Copyright © McGraw-Hill Education. Permission required for reproduction or display.



FSM Example: Danger Sign (US)


- › One input: on/off switch
- › Five outputs: lights
- › When sign is off, no lights
- › When sign is on:

 1. No lights
2. 1 and 2 on
3. 1, 2, 3, and 4 on
4. 1, 2, 3, 4, and 5 on



- › Repeats states 1 to 4 as long as switch is on


Danger Sign: State Diagram

 

- › Four states. Assign a two-bit label to each state.
- › Input: 1 = on, 0 = off. State transitions are labeled with the input that causes that transition.
- › Outputs: 1 bit per light.

Danger Sign: Implementation

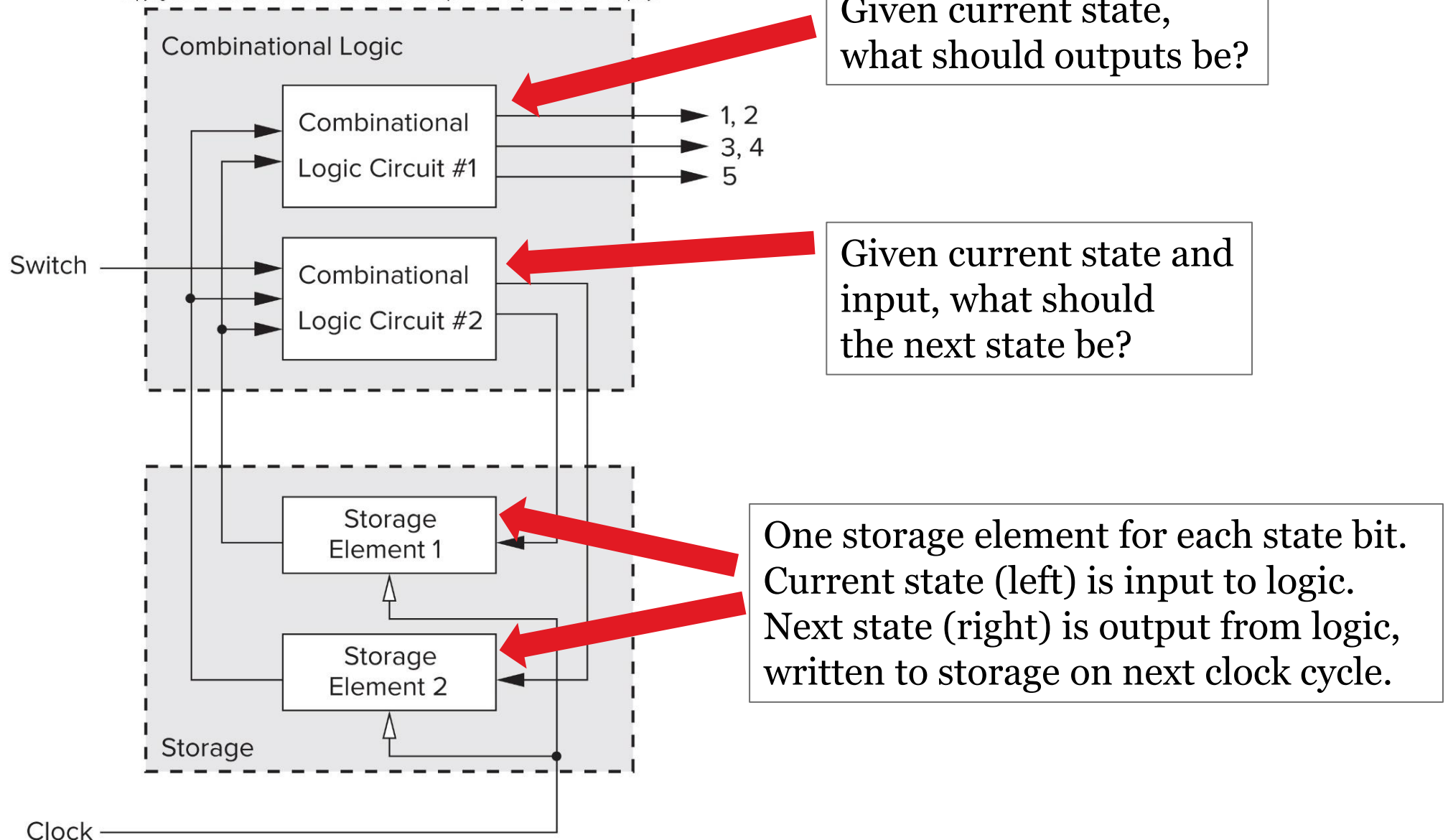Copyright © McGraw-Hill Education. Permission required for reproduction or display.



Danger Sign: Truth Tables

- Two truth tables: one for each combinational logic circuit.
- On left, translate state $S[1:0]$ to output signals:
 $W = \text{lights 1 \& 2}$, $X = \text{lights 3 \& 4}$, $V = \text{light 5}$
- On right, translate input (Switch) and state $S[1:0]$ to next state: $S'[1:0]$


| $S[1:0]$ | W | X | V |
|----------|---|---|---|
| 00 | 0 | 0 | 0 |
| 01 | 1 | 0 | 0 |
| 10 | 1 | 1 | 0 |
| 11 | 1 | 1 | 1 |

| Switch | $S[1:0]$ | $S'[1:0]$ |
|--------|----------|-----------|
| 0 | 00 | 00 |
| 0 | 01 | 00 |
| 0 | 10 | 00 |
| 0 | 11 | 00 |
| 1 | 00 | 01 |
| 1 | 01 | 10 |
| 1 | 10 | 11 |
| 1 | 11 | 00 |

- All information can be read from the **state diagram**



Danger Sign: Combinational Logic

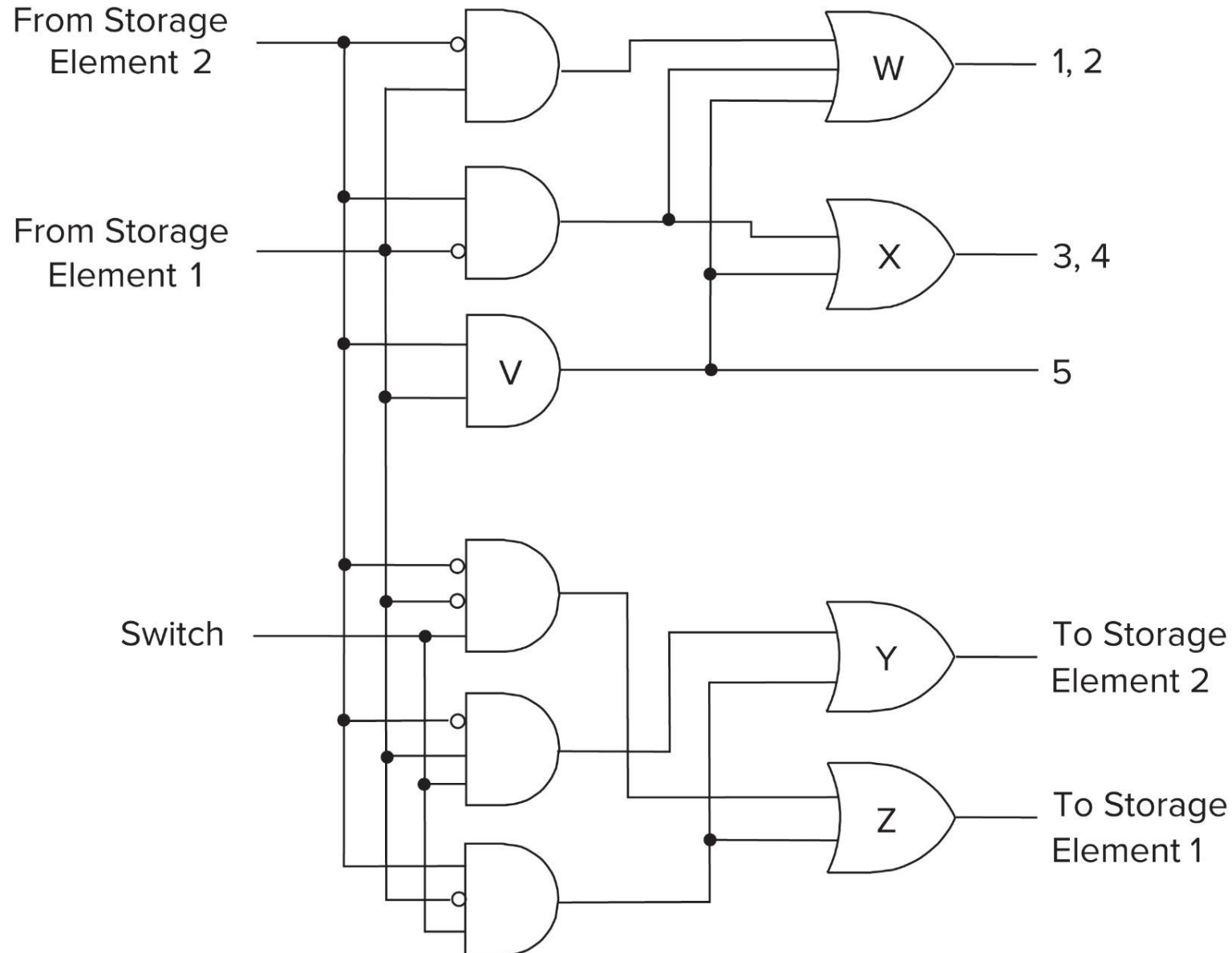Copyright © McGraw-Hill Education. Permission required for reproduction or display.



FSM Summary

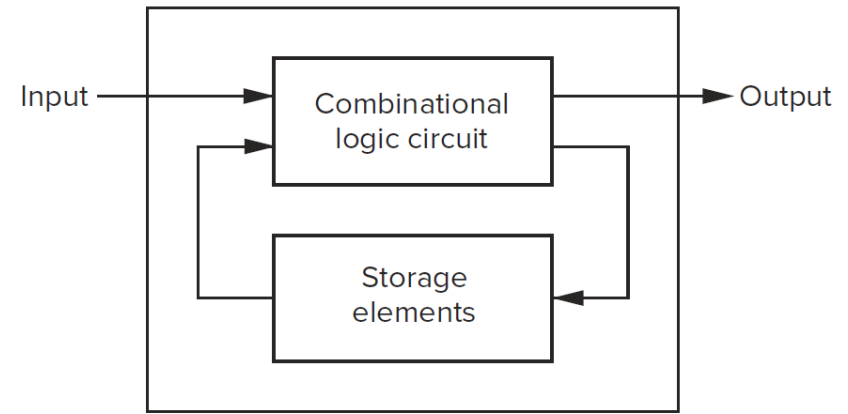 - State diagram, truth tables, and circuit are three different representations of the state machine. Given one, we can easily derive the other two.



| S[1:0] | W | X | V | Switch | S[1:0] | S'[1:0] |
|--------|---|---|---|--------|--------|---------|
| 00 | 0 | 0 | 0 | 0 | 00 | 00 |
| 01 | 1 | 0 | 0 | 0 | 01 | 00 |
| 10 | 1 | 1 | 0 | 0 | 10 | 00 |
| 11 | 1 | 1 | 1 | 0 | 11 | 00 |
| | | | | 1 | 00 | 01 |
| | | | | 1 | 01 | 10 |
| | | | | 1 | 10 | 11 |
| | | | | 1 | 11 | 00 |


Synchronous versus Asynchronous

- › In examples so far, no fixed notion of time.
- › The outputs may occur any time between inputs.
- › This is an **asynchronous** system. The inputs change the output whenever they happen...

- › In a **synchronous** system, state transitions happen at fixed time intervals. At each interval, the input and state determine the transition.

Synchronous versus Asynchronous

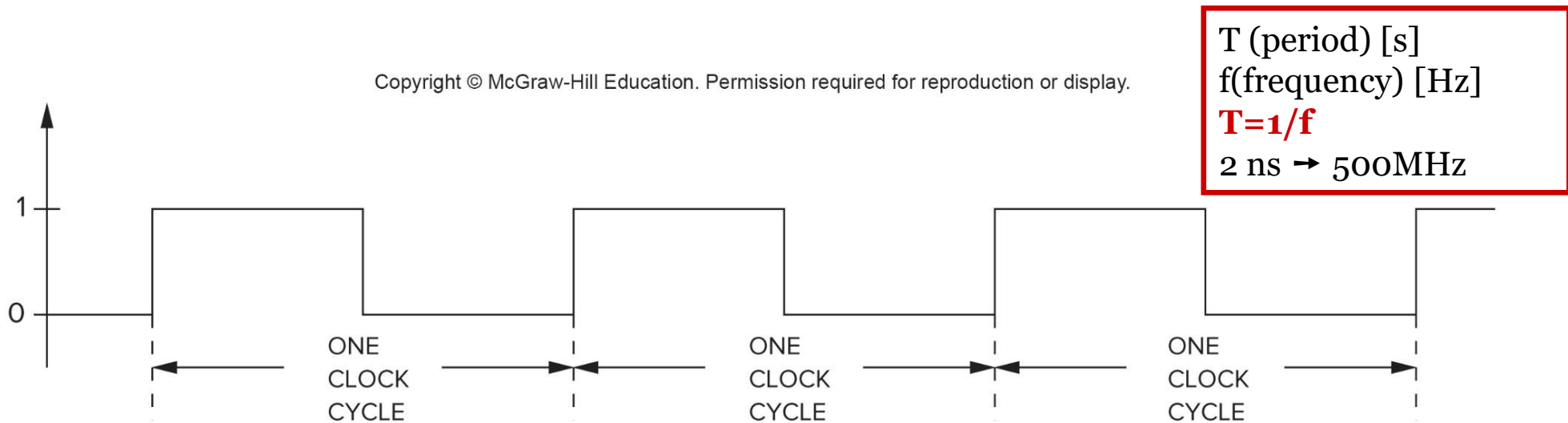- › A **clock signal** is used to trigger the state transitions.
- › For example, a transition happens whenever the clock changes from 0 to 1.



Storage Elements: D-Latch?


- › Suppose we use a D-Latch to store each data bit.
- › We want the new state to be written into the latch each clock cycle. So we can use the **Clock** signal as write-enable (**WE**).
- › **Problem:**
- › As long as $WE = 1$, the new data will change the stored data.
- › This means that we need WE (Clock) to go back to zero **before** the next state is prepared by the logic circuit. Otherwise, we would transition through two or more states in a single clock cycle.
- › **Solution: flip-flop!**

Signal Propagation Delay

- › Propagation delay is the amount of time required after an input signal is applied until the output of the circuit has stabilized to the correct output signal.
- › Each gate adds a short delay to the signal.
- › The longer paths experience larger delays.

 
Example: Asynchronous State Transition

- › In the following example, the initial input is (0,0,0).
- › The input changes to (1,1,1).
- › We expect the same output however, there will be a transient output due to the propagation delay.




D-Latch: Simpler Control for One-Bit Latch (Recap)

 - › D = data input, WE = write enable
- › When WE = 0, latch output does not change (D is irrelevant)
- › When WE = 1, latch output = D



Storage Elements: Flip-flop

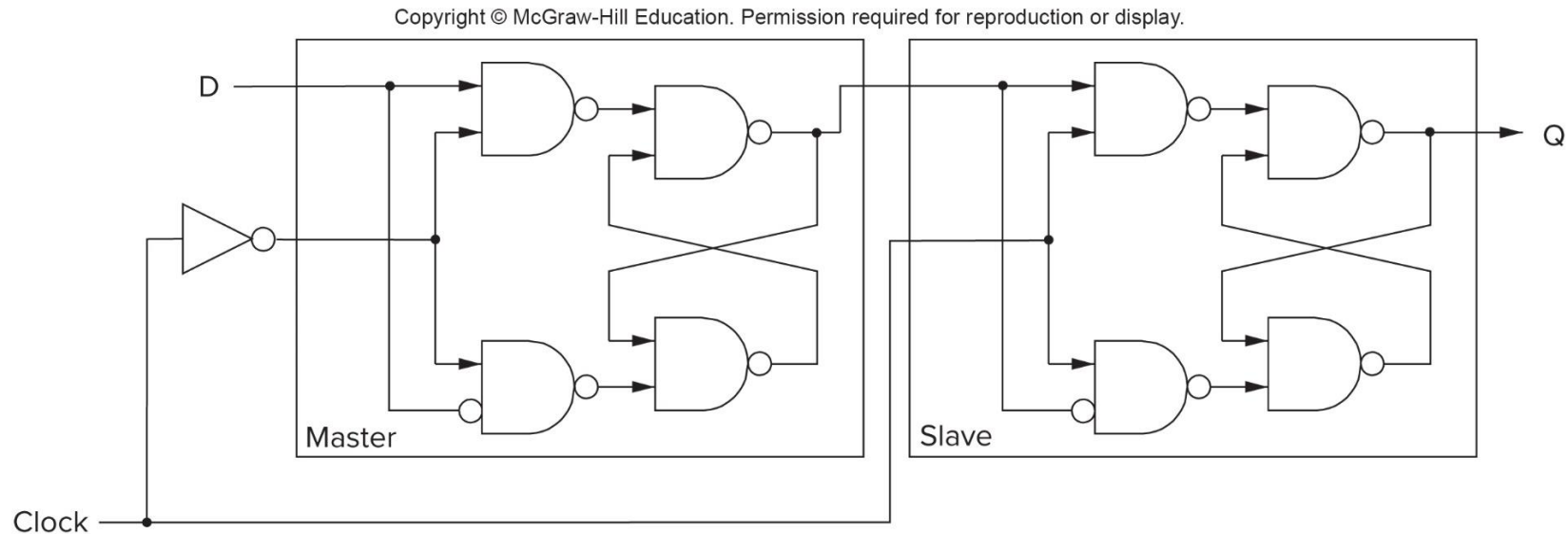- › A flip-flop uses two latches to separate the reading phase and the writing phase of the clock cycle




When Clock = 0 (write phase), new data (D) is stored in the Master latch, but output (Q) **does not change**.

When Clock = 1 (read phase), data from Master is stored into the Slave and the output (Q) **changes** to the new value.

Timing Diagram

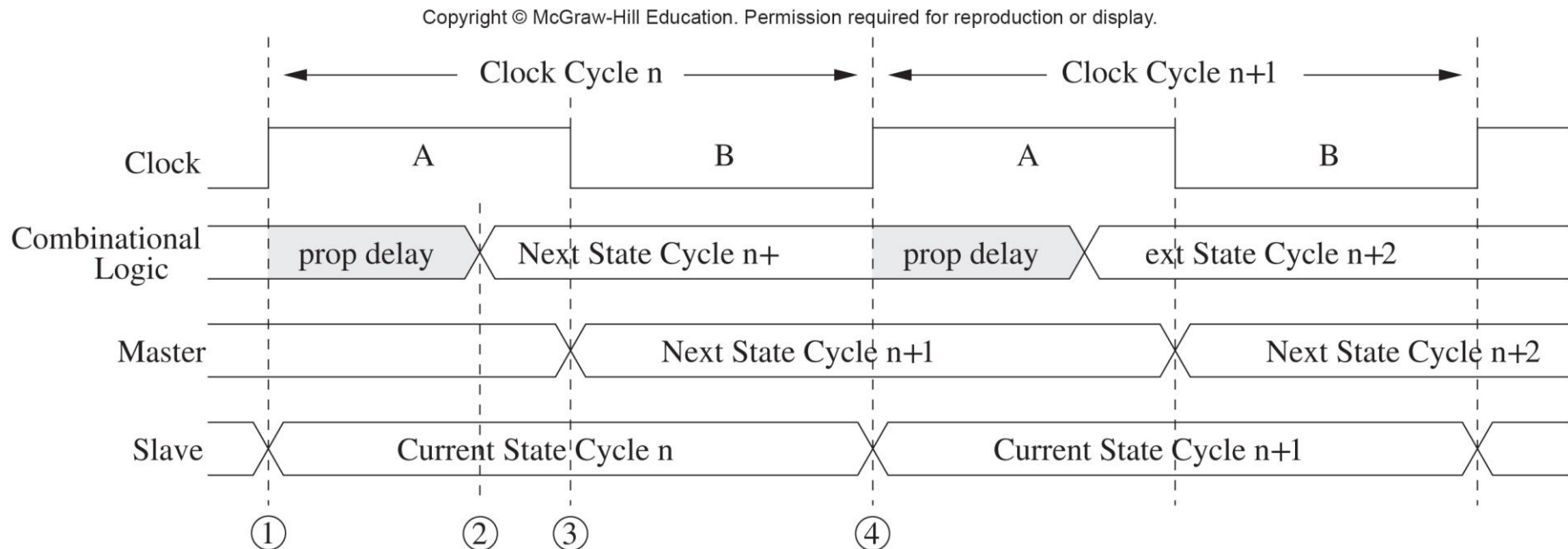
Transistors (logic gates, latches) and wires are not ideal. It takes time for the electrons to do the work or travel.



- As long as worst-case propagation delay through the logic is less than half of the clock cycle, state will properly change each clock cycle.
- Because of this behavior, flip-flop is considered an *edge-triggered* storage element: its state changes on the clock edge. A latch is *level-triggered*, because it changes as long as the WE signal is enabled.

Clock Frequency

› Critical path

 

How fast can the clock be?


FYI: $T = 1/f$

where T is period [s] and f is frequency [Hz]

The period of 1GHz clock signal is 1 ns

Registers

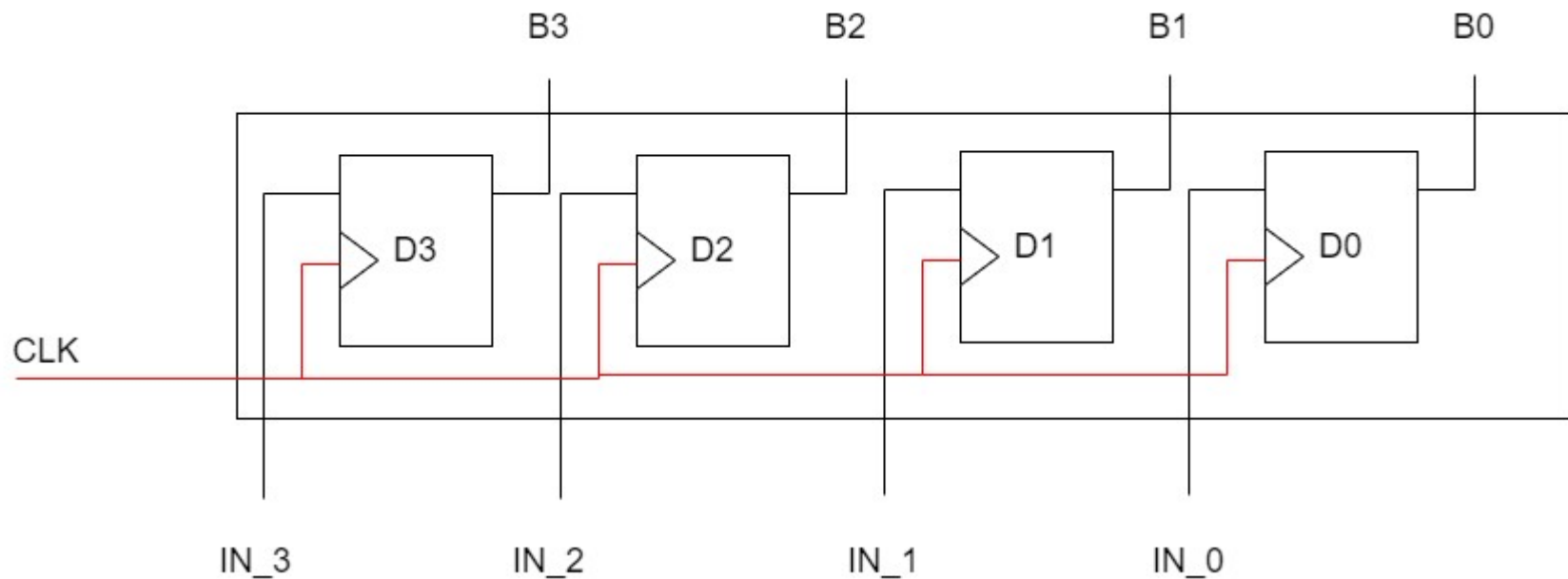
- › Registers are a type of computer memory used by the CPU.
- › It acts like an N-bit memory
- › They can be built out of latches/flip flops






Registers with Load Control

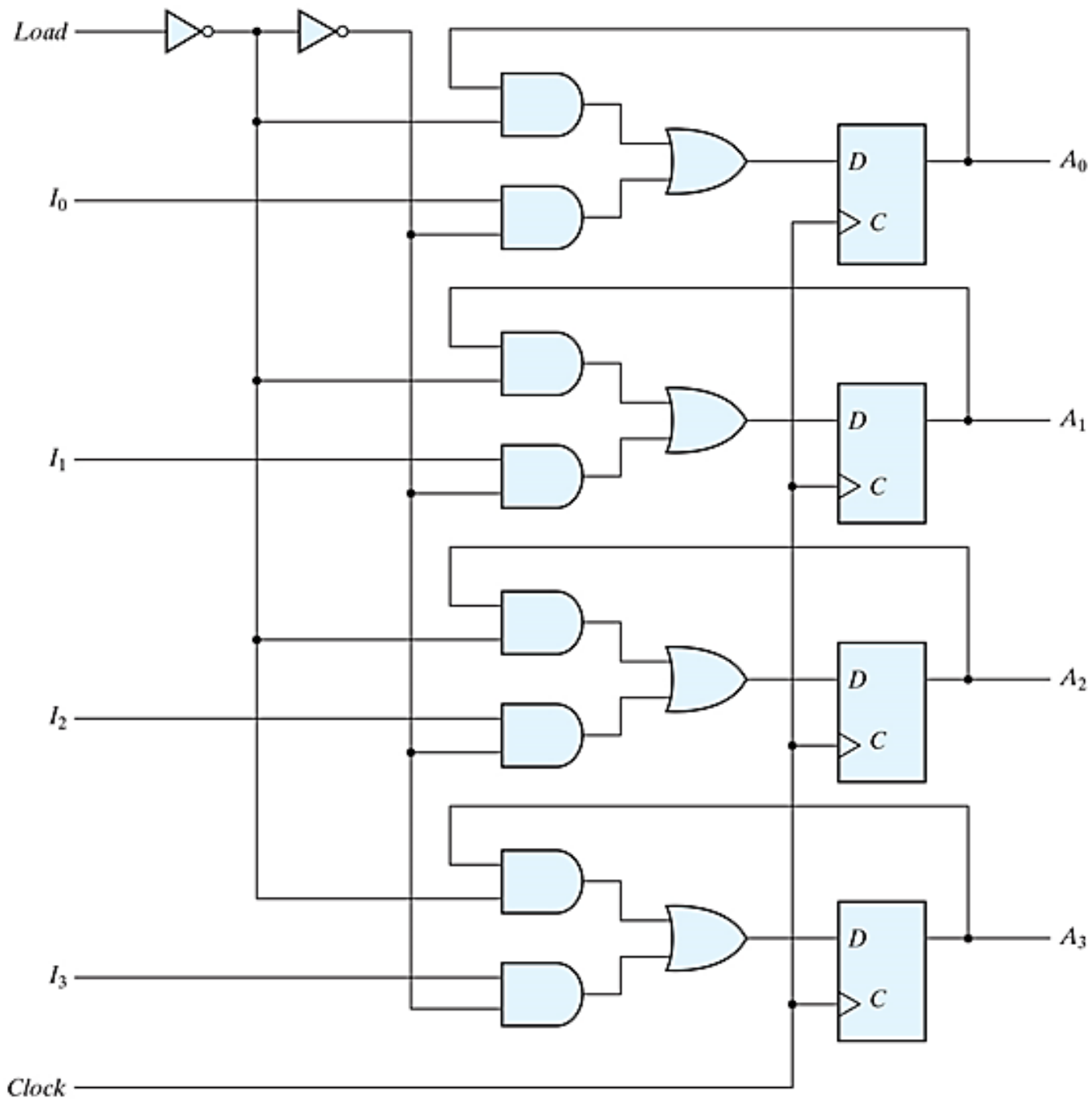- › The input to the memory cells (flip-flops) of a register may change with changes in the outputs of the combinational circuits.
- › To control when data should be loaded into a register, we use a load input




Shift Registers

 - › A register may have only serial inputs, where the input is loaded bit by bit, and is moved from one flip-flop to the next (hence shift registers)
- › Reading the data from these registers is also done serially.
- › These registers are called **serial-in, serial-out, shift registers**.



Serial Transfer

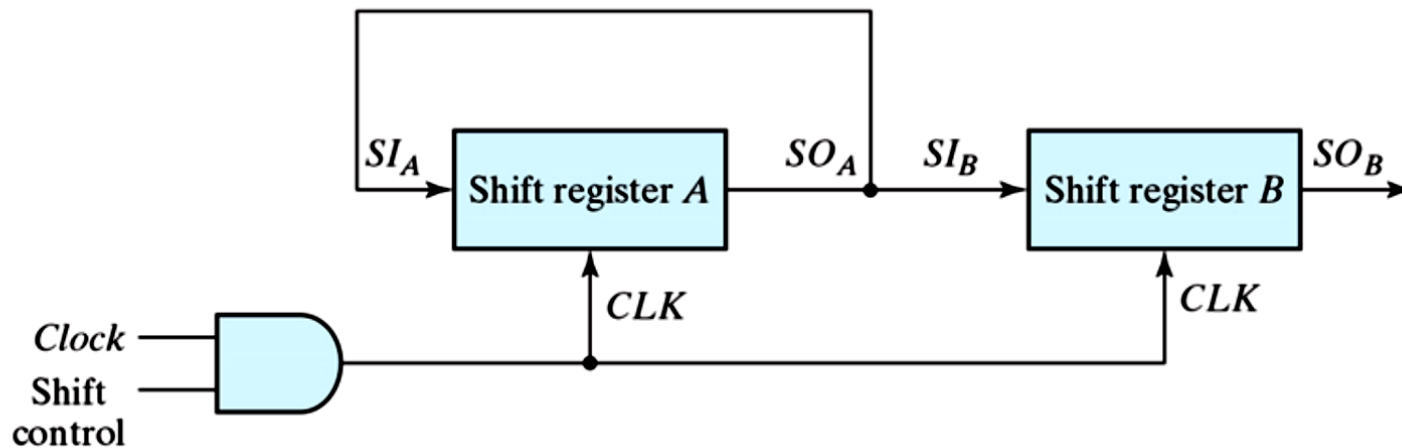
- › The content of a register can be copied into a second register serially.
- › This is called serial transfer operation.



General Shift Registers

- › A general shift register has the capabilities of:
 - Parallel data load
 - Serial data load by
 - Shift to left and insert a bit from right
 - Shift right and insert a bit from left
 - Reset (load logical zero)
 - Preserve current data
- › A 4x1 mux can be used to decide which action should be carried out.

| S1 | S2 | Action |
|----|----|---------------|
| 0 | 0 | Keep Value |
| 0 | 1 | Shift Left |
| 1 | 0 | Shift Right |
| 1 | 1 | Parallel Load |

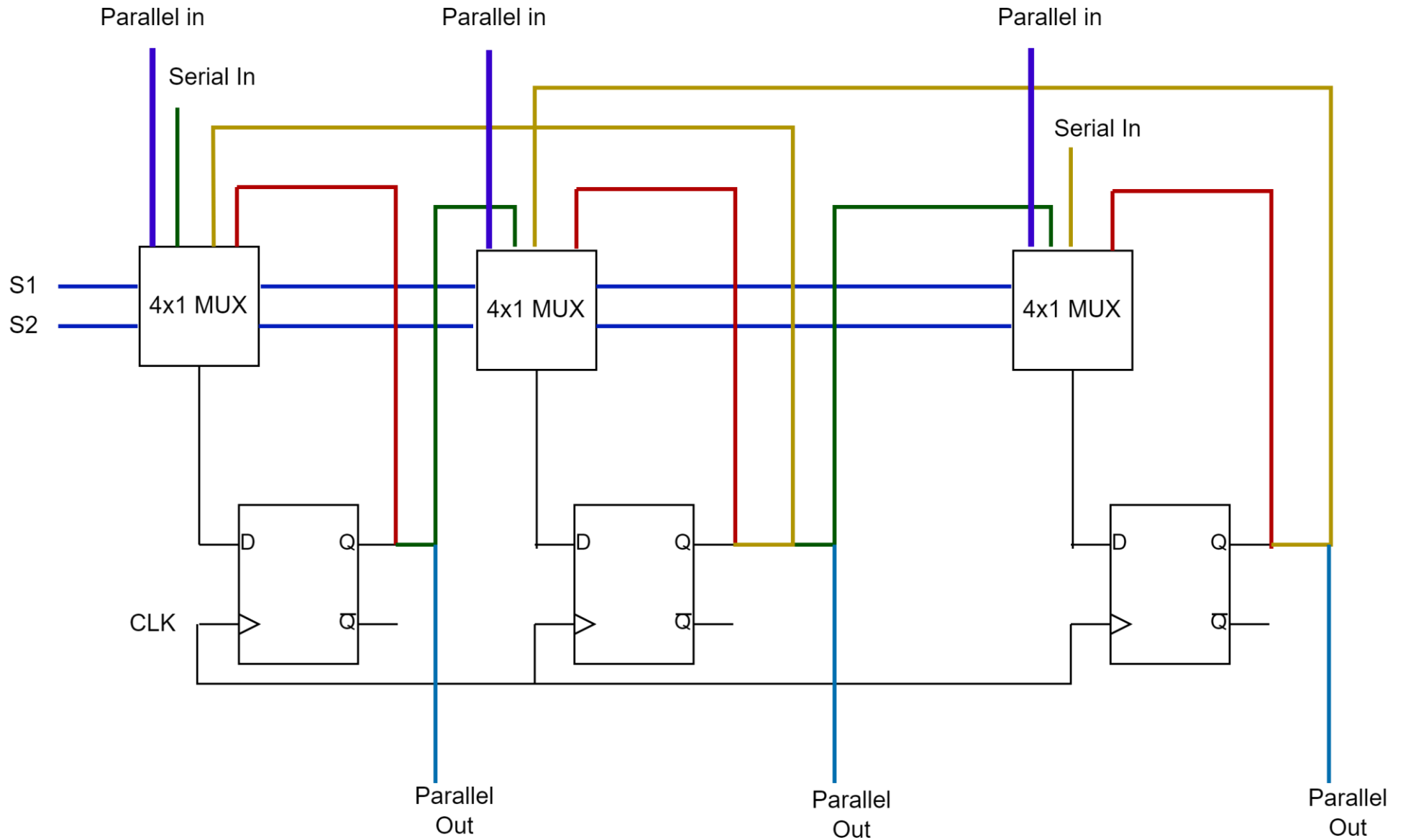




Serial Adder

- › Assume we have two registers A, and B.
- › We want to add the values in these registers, putting the result in register A.
- › We want to use only one full adder, and a flip-flop.

Serial Adder

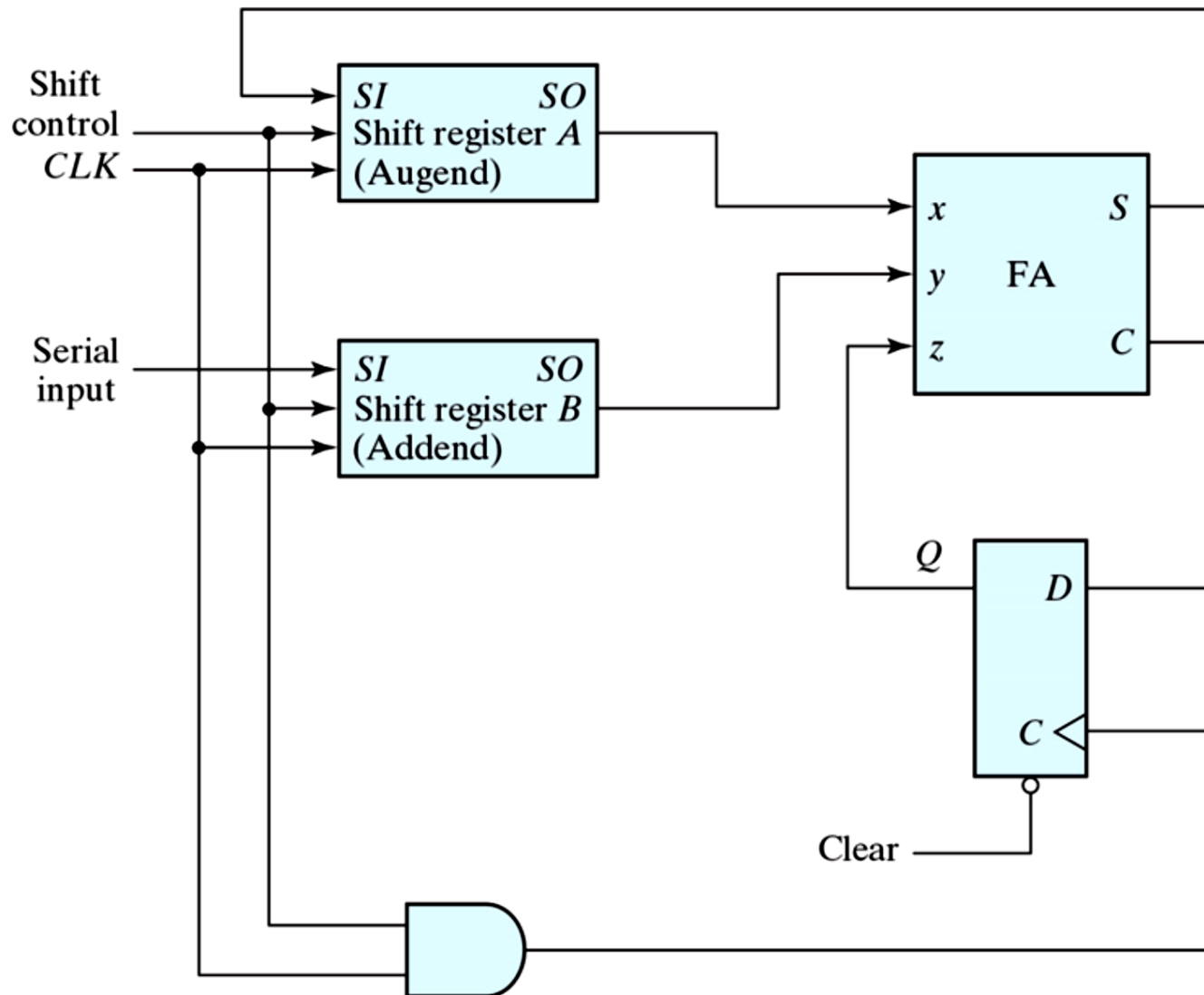




Counters

- › A counter is a sequential circuit to count numbers from zero, to a maximum defined for the circuit.
- › Counters can be designed as synchronous, or asynchronous circuits.
- › Ripple counter is an example of an asynchronous counter.



Ripple Counter

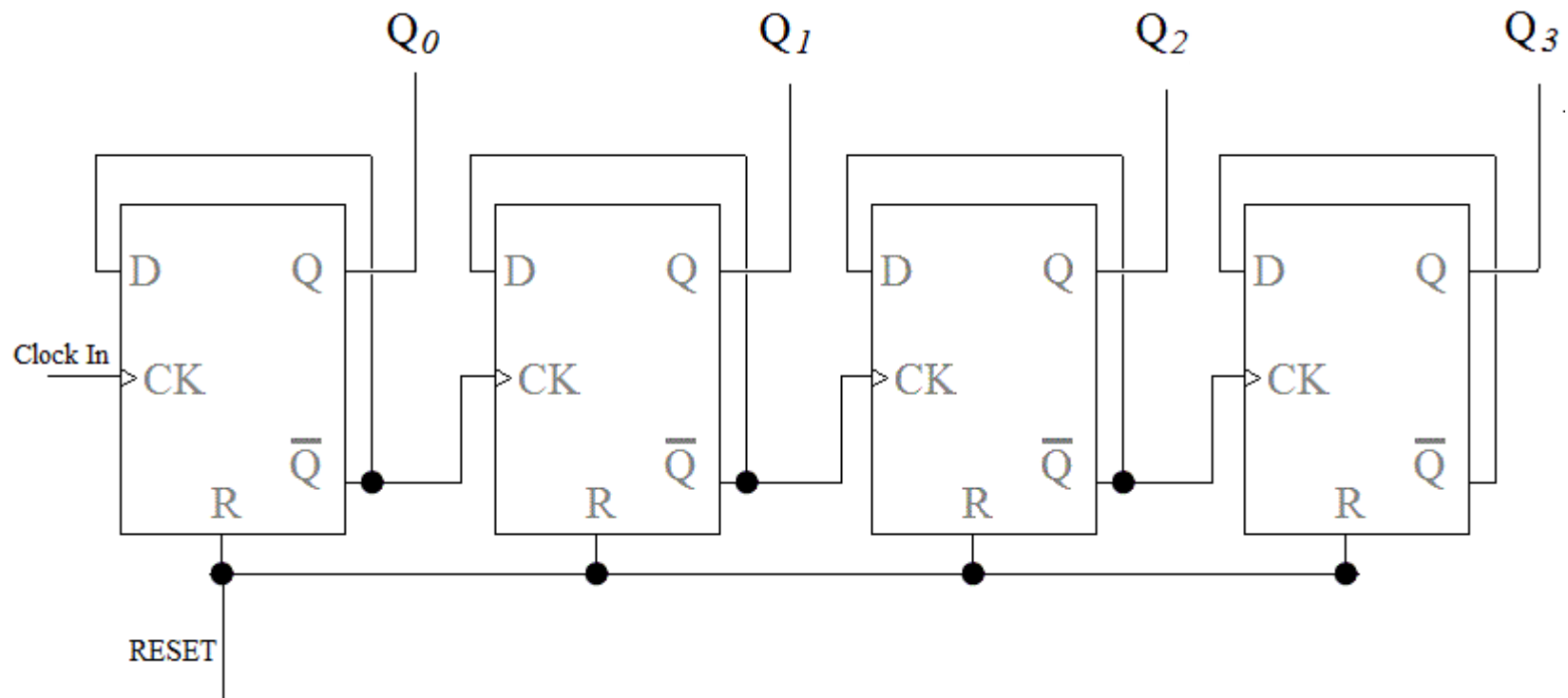

Summary

- › Sequential logic circuits are used to combine the current input and the past output to generate new outputs.
- › The current output is considered as the state of the circuit.
- › Finite State Machine are used to define the transitions from one state to the next based on the given inputs.
- › Synchronized circuits limit the changes in the output to discrete points in time. In this way, the oscillation at the output is prevented.



university of
 groningen

Questions?